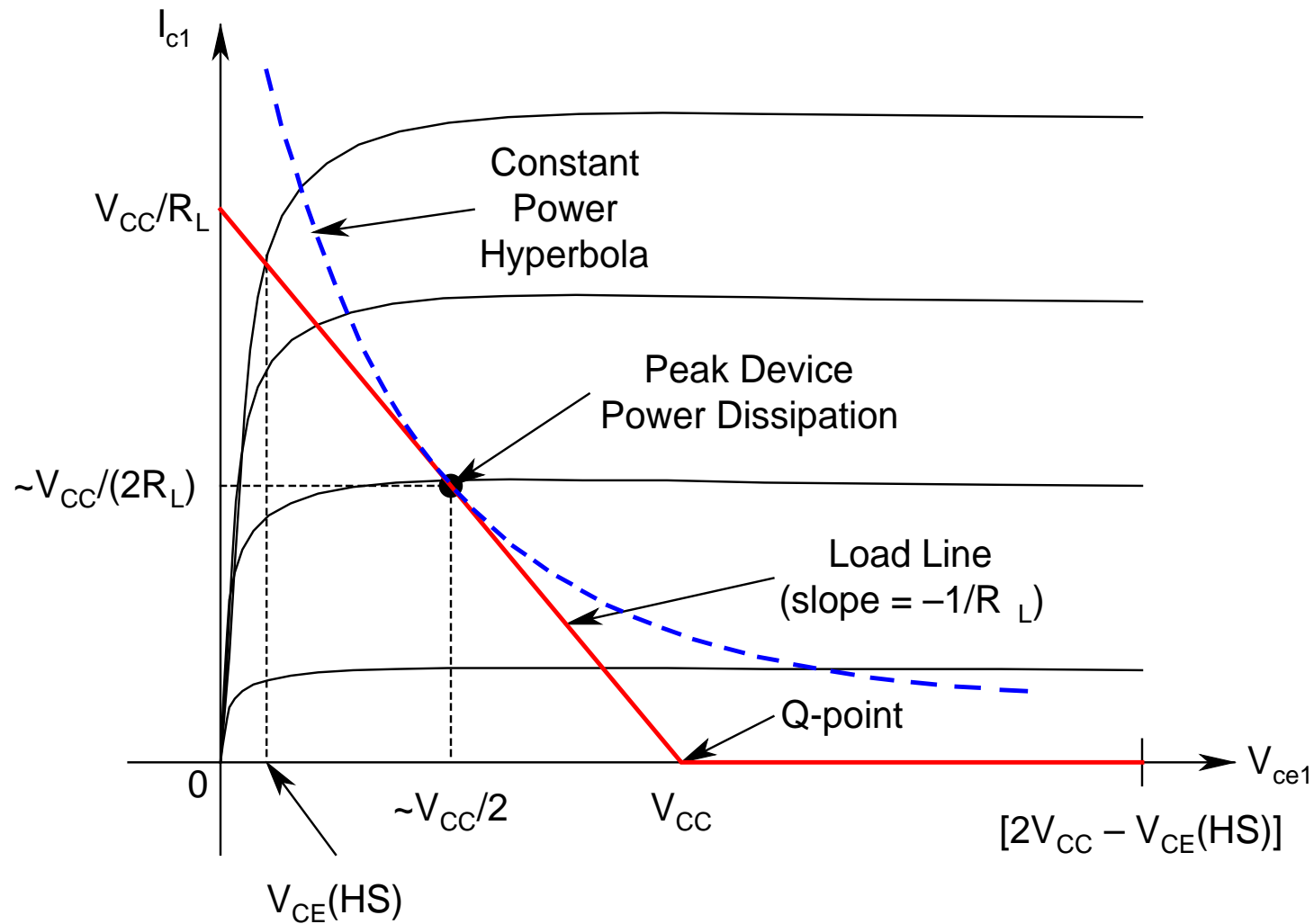


➤ *Transistor Ratings:*

- Specified by *two parameters*:
 - ❖ *Breakdown Voltage*
 - ❖ *Maximum Power Rating*
- *Breakdown Voltage*:
 - ❖ *Maximum positive/negative V_{CE} that can be applied to an npn/pnp BJT*
 - Known as the *Collector-to-Emitter Breakdown Voltage with Base Open* (BV_{CE0})
 - ❖ *Focus on Q_1 (Q_2 will be similar)*
 - ❖ Refer to the diagram in the next slide (*Output characteristic of Q_1 along with the load line*)
 - ❖ In the analysis, the *offset in the VTC*, the *small standby current*, and $V_{CE1}(HS)$ are *neglected*



The Output Characteristic of Q_1 along with the Load Line

- ❖ *At Q-point: $V_o = 0 \Rightarrow V_{ce1} = V_{CC}$*
- ❖ *During positive half cycle:*
 - $V_o(max) \approx V_{CC} \Rightarrow V_{ce1} \approx 0$
 - $\Rightarrow V_{ce1}$ *ranges between 0 and V_{CC} during the positive half cycle*
- ❖ The *slope of the load line* in this part of the characteristic = $-1/R_L$
- ❖ *For negative half cycle, Q_1 cuts off (Q_2 conducts during this period)*
 - $\Rightarrow I_{c1} = 0$ *for V_o ranging between 0 and $-V_{CC}$*
 - $\Rightarrow V_{ce1}(max) = 2V_{CC}$
 - $\Rightarrow BV_{CE0} = 4V_{CC}$ [using a *Safety Factor* (or *Factor of Safety*) of 2]

■ **Maximum Power Rating:**

❖ *Same for both Q_1 and Q_2*

❖ *Average power P_L delivered by Q_1 to R_L during the positive half cycle = area covered under the load line*

$$\Rightarrow P_L = \frac{1}{2} \times V_{CC} \times \frac{V_{CC}}{R_L} = \frac{V_{CC}^2}{2R_L}$$

❖ Refer to the *constant power hyperbola* ($V_{ce1} \times I_{c1}$) shown in the figure

❖ *Maximum power dissipation of Q_1 happens when this hyperbola becomes tangent to the load line, which is right at the middle of the load line*

❖ *Proof:*

Constant power hyperbola (P_1):

$$P_1 = V_{ce1} \times I_{c1} = (V_{CC} - I_{c1} R_L) \times I_{c1} = V_{CC} I_{c1} - I_{c1}^2 R_L$$

Plug $dP_1/dI_{c1} = 0$ to get $I_{c1} = V_{CC}/(2R_L)$

This is the *mid-point of the load line*, with *coordinates* $[V_{CC}/2, V_{CC}/(2R_L)]$

$$\Rightarrow P_{\max} = \frac{V_{CC}^2}{2R_L} \text{ (using a Safety Factor of 2)}$$

❖ There is also *standby power*:

$$P_{\text{Standby}} = V_{CC} \times I_{\text{Standby}}$$

❖ In general, $P_{\max} \gg P_{\text{Standby}}$

❖ Refer to the figure in the next slide

- o V_{ce1} *oscillates between 0 and $2V_{CC}$*
- o I_{c1} *appears only during the positive half cycle, with peak value of V_{CC}/R_L (when $V_{ce1} = 0$)*
- o $P_1 (= V_{ce1} \times I_{c1})$ *oscillates* between 0 and $V_{CC}^2/(4R_L)$ at *twice the frequency* only during the *positive half cycle*