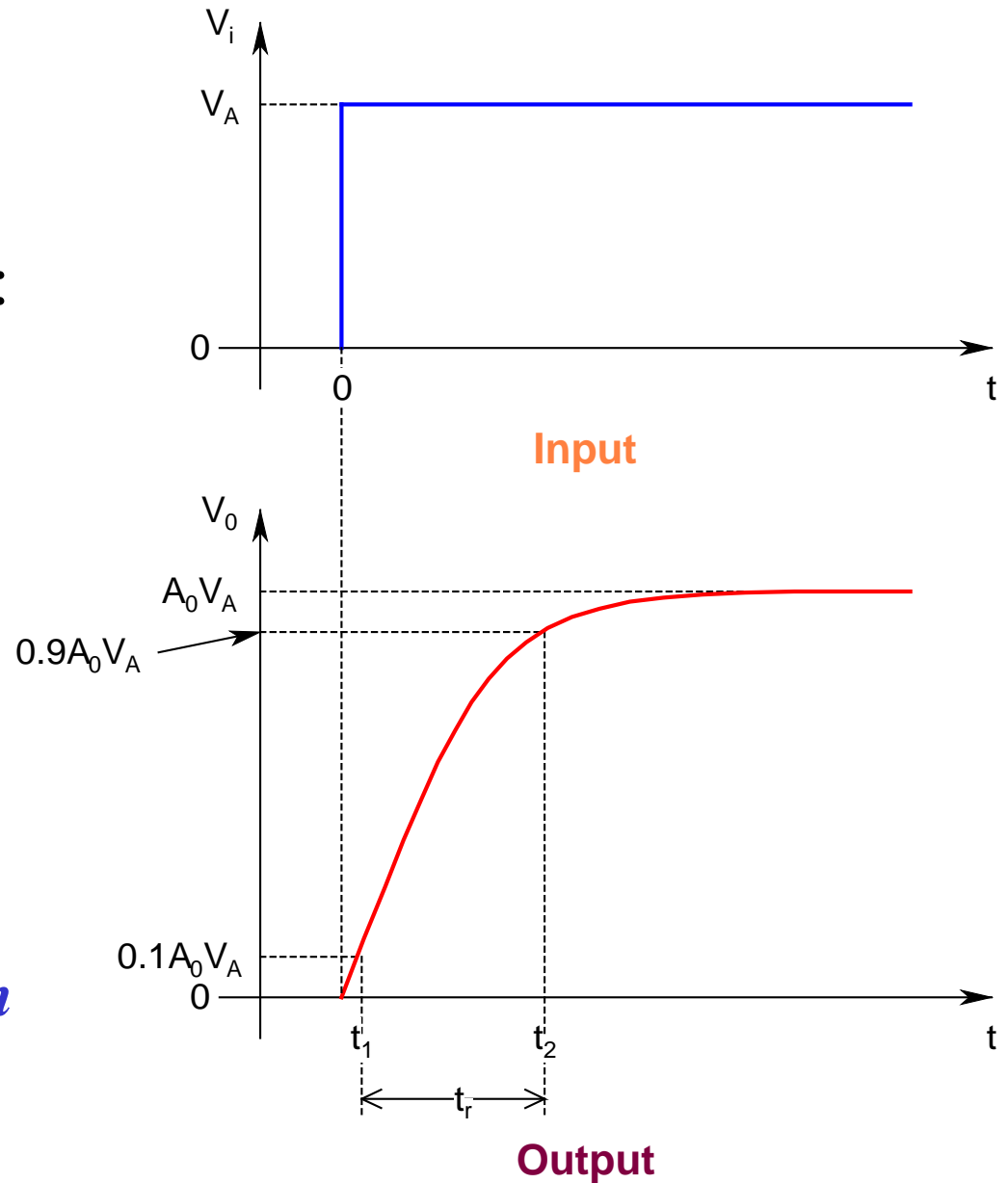


➤ ***Calculation of Rise/Fall Time:***

- *Time taken for the output to rise (fall) from 10% (90%) to 90% (10%)*
- *Can be calculated from the figure*



- *At $t = t_1$:*

$$0.1A_0V_A = A_0V_A[1 - \exp(p_1t_1)]$$

$$\Rightarrow t_1 = \ln(0.9)/p_1$$

- *At $t = t_2$:*

$$0.9A_0V_A = A_0V_A[1 - \exp(p_1t_2)]$$

$$\Rightarrow t_2 = \ln(0.1)/p_1$$


- Thus, the *rise time*:

$$t_r = t_2 - t_1 = -2.2/p_1 = 2.2/\omega_H = 0.35/f_H$$

- Hence, *higher the f_H , smaller the t_r*
- *The same expression holds for the fall time (t_f) as well*

- Thus, circuits having *high bandwidth* under *sinusoidal excitation* (*analog domain*), will also have *superb switching characteristics* under *square-wave excitation* (*digital domain*)
- Under *square-wave excitation*, *due to t_r/t_f* , *enough time should be provided for the transient in the output to get completed*
- *Rule of Thumb*:
 - *At least 5 time constants should be allowed for each rising and falling transient*
 - This determines the *maximum allowable frequency* of the *input pulse train*:

$$f_{\max} = 1/T_{\min} \approx 1/(10\tau) = \omega_H/10 = |p_1|/10$$

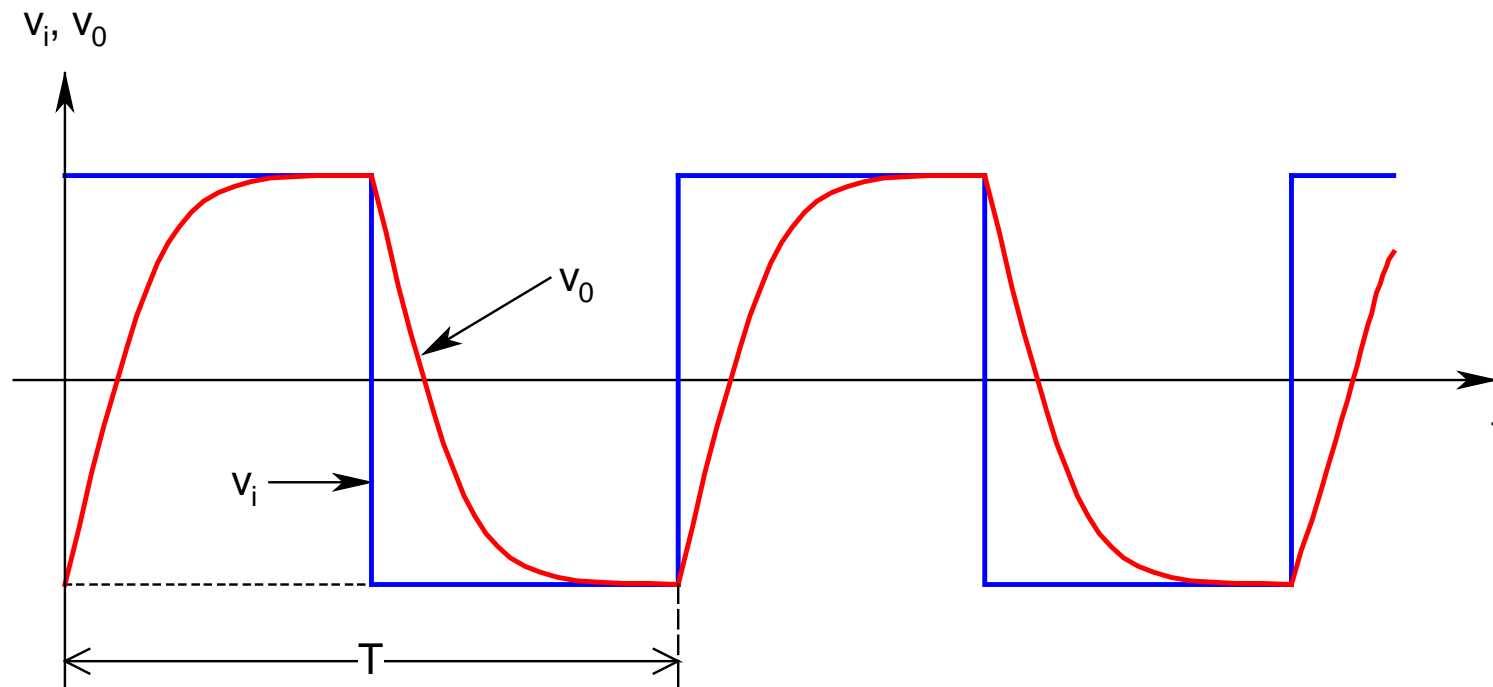

Effect of t_r/t_f on the Output for Square-Wave Excitation

- *As $f \uparrow$, $T \downarrow$, V_0 first starts to become triangular (incomplete transient), then the amplitude starts to drop, and eventually drops to zero (no output at all!)*