

ESC201T : Introduction to Electronics

Tutorial Quiz : MQ1 (11th sept.)

Determine power dissipated/generated in dependent current source shown below. Write your answer with all relevant steps on a piece of paper, take a photograph and upload it on mooKIT. If that does not work, send email only to your tutor. Try to send email within time.

