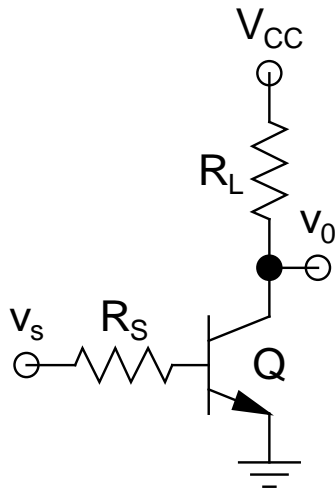


➤ *Zero-Value Time Constant (ZVTC)*


*Technique:*

- *The easiest one*
- *Information regarding only the DP*
- *Suppresses information about all other poles and zeros of the system*
- *Reasonable accuracy*
- *Underestimates  $f_H$  slightly (better than overestimating and not achieving it!)*
- *Based on heuristic*
- *Similar to the IVTC technique, based on an algorithm*

- *Exact Analysis of a CE Stage:*



ac Schematic

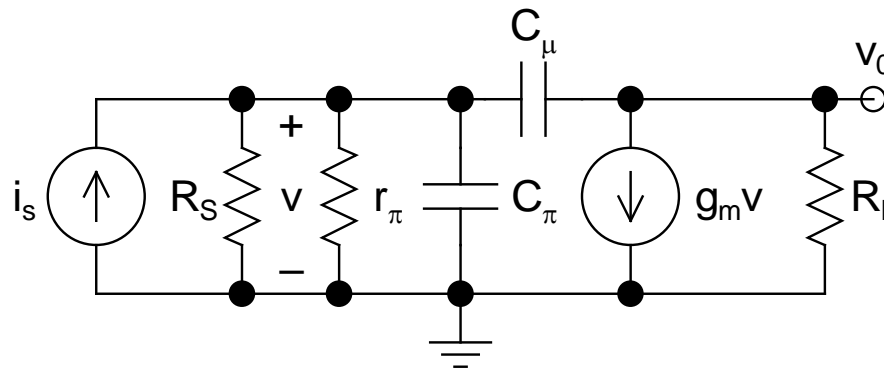

High-Frequency Equivalent

- *Biasing circuits omitted for simplicity*
- *Converted input  $v_s$  to its Norton equivalent*

➤ **KCL at input node** (using **Laplace operator**  $s = j\omega$  and  $R = R_S || r_\pi$ ):

$$\begin{aligned} i_s &= v/R + sC_\pi v + sC_\mu(v - v_0) \\ &= [1/R + s(C_\pi + C_\mu)]v - sC_\mu v_0 \end{aligned}$$

➤ **KCL at output node:**

$$sC_\mu(v_0 - v) + g_m v + v_0/R_L = 0$$

$$\Rightarrow v = -\frac{1/R_L + sC_\mu}{g_m - sC_\mu} v_0$$

$$\Rightarrow \frac{v_0}{i_s}(s) = -\frac{R_L R (g_m - sC_\mu)}{1 + s(R_L C_\mu + RC_\mu + RC_\pi + g_m R_L RC_\mu) + s^2 R_L RC_\pi C_\mu}$$

➤ Thus, the *voltage gain*:

$$A_v(s) = \frac{V_0}{V_s} = -\frac{g_m R_L R}{R_s} \frac{(1 - sC_\mu / g_m)}{1 + sa + s^2 R_L R C_\pi C_\mu} \quad (1)$$

$$a = R_L C_\mu + R(C_\pi + C_\mu) + g_m R_L R C_\mu$$

➤ Hence, the circuit has *one zero* and *two poles*

$$\Rightarrow A_v(s) = A_{v0} \frac{(1 - s/z_1)}{(1 - s/p_1)(1 - s/p_2)} \quad (2)$$

$$\begin{aligned} A_{v0} &= \textit{midband gain} = -g_m R_L R / R_s \\ &= -g_m R_L r_\pi / (r_\pi + R_s) \end{aligned}$$

- $z_1 (= g_m/C_\mu)$ : *positive real zero*
- The *frequency* corresponding to  $z_1$  occurs at  $z_1/(2\pi)$ , which is *extremely high*, and generally, is *not of much consequence*
- *Computation of the two poles  $p_1$  and  $p_2$  is slightly more tricky*
- From Eqs.(1) and (2), it is obvious that *both  $p_1$  and  $p_2$  are real and negative*

- To find these, *write the denominator* of Eq.(1) as:

$$\begin{aligned} D(s) &= (1 - s/p_1)(1 - s/p_2) \\ &= 1 - s(1/p_1 + 1/p_2) + s^2/(p_1 p_2) \end{aligned} \quad (3)$$

- *Matching coefficients* with Eq.(2), we can get  $p_1$  and  $p_2$ , however, the *resulting algebra* will become *extremely tedious*
- Hence, we invoke the *Dominant Pole Approximation* (DPA)

➤ **DPA:**

- The *smallest pole* [*Dominant Pole* (DP)] is *at least 10 times away from its nearest pole*
- This is an *excellent approximation for practical analog circuits*

➤ *Apply this approximation* and *assume  $p_1$  to be the DP* and *at least 10 times away from  $p_2$*  [*Non-Dominant Pole* (NDP)]

➤ The *pole frequencies* are  $|p_1|/(2\pi)$  and  $|p_2|/(2\pi)$

➤ *Note*:  $|p_1|/(2\pi)$  is the *Upper Cutoff Frequency* ( $f_H$ )