

All BJTs in the circuit shown are identical with $(\beta, V_A) \rightarrow \infty$ [for parts a)-d)].

- a) Show that I_0 is a function only of V_{CC} and R_E , if $R_1 = R_2$. 4
- b) If $I_0 = I_1$, how is R_E related to R_1 (or R_2 , since $R_1 = R_2$)? 2
- c) If $V_{CC} = 5$ V, determine $R_1 (= R_2)$ and R_E to give $I_0 = 1$ mA. 2
- d) What is $V_{0,min}$? Is the value acceptable to you? Comment. 2
- e) *Only for this part*, assuming $\beta = 100$, $V_A = 100$ V, I_0 and I_1 remain at 1 mA, and using the values of $R_1 (= R_2)$ and R_E calculated in part c), estimate the output resistance R_0 . 5

